 


Basic Logic Gates

Md Saeed Siddik

Assistant Professor,
IIT Dhaka University




Basic Logic Gates and Basic Digital Design



- **NOT, AND, and OR Gates**
- NAND and NOR Gates
- DeMorgan's Theorem
- Exclusive-OR (XOR) Gate
- Multiple-input Gates

NOT Gate -- Inverter

 


X	Y
0	1
1	0

NOT




- $Y = \sim X$ (Verilog)
- $Y = !X$ (ABEL)
- $Y = \mathbf{not} \ X$ (VHDL)
- $Y = X'$
- $Y = \neg X$
- $Y = \overline{X}$ (textbook)
- $\mathbf{not}(Y, X)$ (Verilog)

NOT

 

X	$\sim X$	$\sim\sim X$
0	1	0
1	0	1

AND Gate

 


X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

AND



- $X \ \& \ Y$ (Verilog and ABEL)
- $X \ \mathbf{and} \ Y$ (VHDL)
- $X \ \wedge \ Y$
- $X \ \cap \ Y$
- $X \ * \ Y$
- XY (textbook)
- $\mathbf{and}(Z, X, Y)$ (Verilog)

OR Gate

 

$$Z = X \mid Y$$

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

OR



- $X \mid Y$ (Verilog)
- $X \# Y$ (ABEL)
- $X \text{ **or** } Y$ (VHDL)
- $X + Y$ (textbook)
- $X \vee Y$
- $X \cup Y$
- **or**(Z, X, Y) (Verilog)

Basic Logic Gates and Basic Digital Design




- NOT, AND, and OR Gates
- **NAND and NOR Gates**
- DeMorgan's Theorem
- Exclusive-OR (XOR) Gate
- Multiple-input Gates

NAND Gate



NAND

 


X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

$$Z = \sim (X \& Y)$$

nand(Z, X, Y)

NAND Gate

 


X	Y	W	Z
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

$$W = X \& Y$$

$$Z = \sim W = \sim (X \& Y)$$

NOR Gate

 


$$Z = \sim (X \mid Y)$$

nor(Z, X, Y)

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0

NOR Gate

 

X	Y	W	Z
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

$$W = X \mid Y$$


$$Z = \sim W = \sim (X \mid Y)$$

Basic Logic Gates and Basic Digital Design




- NOT, AND, and OR Gates
- NAND and NOR Gates
- **DeMorgan's Theorem**
- Exclusive-OR (XOR) Gate
- Multiple-input Gates

NAND Gate

 

=

 

$$Z = \sim (X \ \& \ Y)$$

$$Z = \sim X \mid \sim Y$$

X	Y	W	Z
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

X	Y	$\sim X$	$\sim Y$	Z
0	0	1	1	1
0	1	1	0	1
1	0	0	1	1
1	1	0	0	0


De Morgan's Theorem-1



$$\sim (X \ \& \ Y) \ = \ \sim X \ | \ \sim Y$$


- NOT all variables
- Change & to | and | to &
- NOT the result

NOR Gate

 

$$Z = \sim (X \mid Y)$$

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0

 

$$Z = \sim X \ \& \ \sim Y$$

X	Y	$\sim X$	$\sim Y$	Z
0	0	1	1	1
0	1	1	0	0
1	0	0	1	0
1	1	0	0	0

De Morgan's Theorem-2



$$\sim (X \mid Y) = \sim X \ \& \ \sim Y$$


- NOT all variables
- Change & to | and | to &
- NOT the result

Basic Logic Gates and Basic Digital Design



- NOT, AND, and OR Gates
- NAND and NOR Gates
- DeMorgan's Theorem
- **Exclusive-OR (XOR) Gate**
- Multiple-input Gates

Exclusive-OR Gate

 


X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

XOR



- $X \wedge Y$ (Verilog)
- $X \$ Y$ (ABEL)
- $X @ Y$
- $X \oplus Y$ (textbook)
- **xor**(Z, X, Y) (Verilog)

Exclusive-NOR Gate

 

$$Z = \sim (X \wedge Y)$$

$$Z = X \sim \wedge Y$$

$$\mathbf{xnor}(Z, X, Y)$$

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1

XNOR







- $X \sim^{\wedge} Y$ (Verilog)
- $!(X \$ Y)$ (ABEL)
- $X @ Y$
- $X \odot Y$
- **xnor**(Z, X, Y) (Verilog)

Basic Logic Gates and Basic Digital Design











- NOT, AND, and OR Gates
- NAND and NOR Gates
- DeMorgan's Theorem
- Exclusive-OR (XOR) Gate
- **Multiple-input Gates**

    Multiple-input Gates

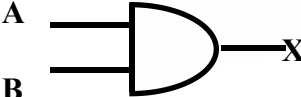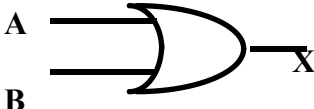

COMBINATIONAL GATES

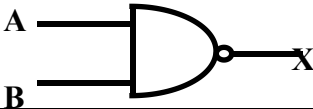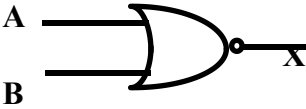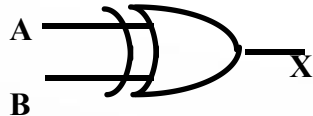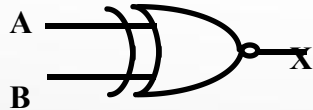Name	Symbol	Function	Truth Table															
AND		$X = A \cdot B$ or $X = AB$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	0	0	1	0	1	0	0	1	1	1
A	B	X																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$X = A + B$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	1
A	B	X																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
I		$X = A'$	<table><tr><th>A</th><th>X</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	A	X	0	1	1	0									
A	X																	
0	1																	
1	0																	
Buffer		$X = A$	<table><tr><th>A</th><th>X</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	A	X	0	0	1	1									
A	X																	
0	0																	
1	1																	
NAND		$X = (AB)'$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	1	1	0	1	1	1	0
A	B	X																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$X = (A + B)'$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	0
A	B	X																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
XOR Exclusive OR		$X = A \oplus B$ or $X = A'B + AB'$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	0
A	B	X																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
XNOR Exclusive NOR or Equivalence		$X = (A \oplus B)'$ or $X = A'B' + AB$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	1
A	B	X																
0	0	1																
0	1	0																
1	0	0																
1	1	1																



<https://logic.ly/demo/>

Live demo



BOOLEAN ALGEBRA

Boolean Algebra



Boolean Algebra



- Algebra with Binary(Boolean) Variable and Logic Operations
- Boolean Algebra is useful in Analysis and Synthesis of Digital Logic Circuits
- Input and Output signals can be represented by Boolean Variables
- Terminology:
 - *Literal*: A variable or its complement
 - *Product term*: literals connected by \cdot
 - *Sum term*: literals connected by $+$

Boolean Algebra Properties



Let X : boolean variable, $0, 1$: constants

1. $X + 0 = X$ -- Zero Axiom
2. $X \cdot 1 = X$ -- Unit Axiom
3. $X + 1 = 1$ -- Unit Property
4. $X \cdot 0 = 0$ -- Zero Property

Boolean Algebra Properties (cont.)



Let X : boolean variable, $0, 1$: constants

5. $X + X = X$ -- Idempotence

6. $X \cdot X = X$ -- Idempotence

7. $X + X' = 1$ -- Complement

8. $X \cdot X' = 0$ -- Complement

9. $(X')' = X$ -- Involution

Algebraic Manipulation

- Boolean algebra is a useful tool for simplifying digital circuits.
- Why do it? Simpler can mean cheaper, smaller, faster.
- Example: Simplify $F = x'yz + x'yz' + xz$.

$$\begin{aligned} F &= x'yz + x'yz' + xz \\ &= x'y(z+z') + xz \\ &= x'y \cdot 1 + xz \\ &= x'y + xz \end{aligned}$$

Algebraic Manipulation (cont.)



- Example: Prove

$$x'y'z' + x'yz' + xyz' = x'z' + yz'$$

- **Proof:**

$$\begin{aligned} x'y'z' + x'yz' + xyz' &= x'y'z' + x'yz' + x'yz' + xyz' \\ &= x'z'(y' + y) + yz'(x' + x) \\ &= x'z' \cdot 1 + yz' \cdot 1 \\ &= x'z' + yz' \end{aligned}$$

Truth Table




The most elementary specification of the function of a Digital Logic Circuit is the Truth Table

Table that describes the Output Values for all the combinations of the Input Values, called *MINTERMS*


- n input variables $\rightarrow 2^n$ minterms

LOGIC CIRCUIT DESIGN

 


x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$F = x + y'z$$

 

Combinational Circuits

 Consider the following Boolean expression $A(B + C)$



A	B	C	$B + C$	$A(B + C)$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

Theorem to Prove

$$(A+B) \cdot (A+C) = A+(B \cdot C) \text{ (Distributive Law)}$$



A	B	C	A+B	A+C	(A+B) · (A+C)	B · C	A+(B · C)
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

Daily Life Example: Choosing a Movie



- You're trying to decide what movie to watch tonight. You have three criteria:
 - A: The movie is a Comedy
 - B: The movie has good reviews
 - C: Your friend is available to watch
- Let's say you decide on the following rule for watching a movie:

"We watch a movie if it's a Comedy AND has good reviews, OR if my friend is available."

Boolean algebra



- In Boolean algebra, this would look like: $(A \times B) + C$

A (Comedy)	B (Good Reviews)	C (Friend Available)	A · B (Comedy AND Good Reviews)	(A · B) + C (Watch Movie?)
0 (No)	0 (No)	0 (No)	0	0 (No Movie)
0 (No)	0 (No)	1 (Yes)	0	1 (Watch Movie)
0 (No)	1 (Yes)	0 (No)	0	0 (No Movie)
0 (No)	1 (Yes)	1 (Yes)	0	1 (Watch Movie)
1 (Yes)	0 (No)	0 (No)	0	0 (No Movie)
1 (Yes)	0 (No)	1 (Yes)	0	1 (Watch Movie)
1 (Yes)	1 (Yes)	0 (No)	1	1 (Watch Movie)
1 (Yes)	1 (Yes)	1 (Yes)	1	1 (Watch Movie)



End of this Lecture